

Introduction to Computer Engineering – EECS 203

<http://ziyang.eecs.northwestern.edu/~dickrp/eecs203/>

Instructor: Robert Dick
Office: L477 Tech
Email: dickrp@northwestern.edu
Phone: 847-467-2298

TA: Neal Oza
Office: Tech. Inst. L375
Phone: 847-467-0033
Email: nealoza@u.northwestern.edu

TT: David Bild
Office: Tech. Inst. L470
Phone: 847-491-2083
Email: d-bild@northwestern.edu



NORTHWESTERN
UNIVERSITY

Outline

1. Memory
2. Latches
3. Clocks
4. Homework


Memory

- Combinational logic outputs a function of inputs, only
- Sequential logic outputs a function of inputs and *state*
- State is remembered
- Consider a sequential vending machine

Flip-flop introduction


- Stores, and outputs, a value
- Puts a special clock signal in charge of timing
- Allows output to change in response to clock transition
- More on this later
 - Timing and sequential circuits

Feedback and memory

 

- Feedback is the root of memory
- Can compose a simple loop from NOT gates

Feedback and memory

 


- Feedback is the root of memory
- Can compose a simple loop from NOT gates
- However, there is no way to switch the value

Outline


1. Memory
2. Latches
3. Clocks
4. Homework

TG and NOT-based memory

 


- Can break feedback path to load new value
- However, potential for timing problems

Ring oscillators


 


Like pulse shaping circuits with memory


Ring oscillators

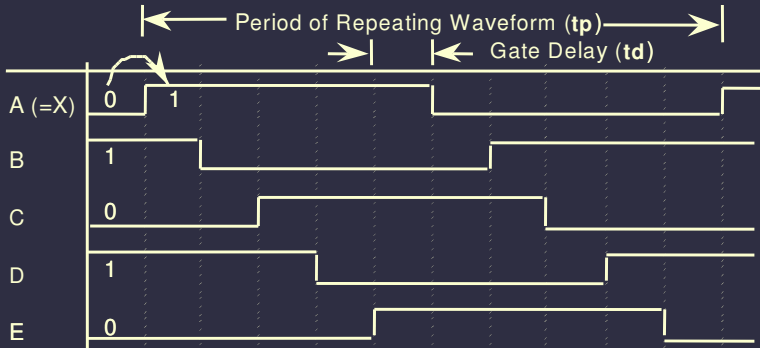

Reset/set latch

  


Reset/set timing

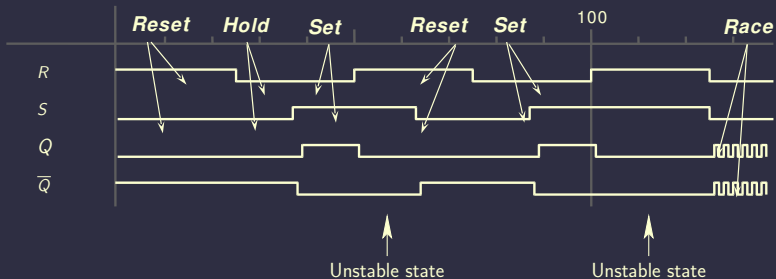

RS latch state diagram


output = $Q \bar{Q}$
input = $R S$

 

Outline


1. Memory
2. Latches
3. Clocks
4. Homework

Clocking terms

 


- Clock – Rising edge, falling edge, high level, low level, period
- Setup time: Minimum time before clocking event by which input must be stable (T_{SU})
- Hold time: Minimum time after clocking event for which input must remain stable (T_H)
- Window: From setup time to hold time

Gated RS latch

 

Gated RS latch

 

Memory element properties

Type	Inputs sampled	Outputs valid
Unclocked latch	Always	LFT
Level-sensitive latch	Clock high (T_{SU} to T_H) around falling clock edge	LFT
Edge-triggered flip-flop	Clock low-to-high transition (T_{SU} to T_H) around rising clock edge	Delay from rising edge

Clocking conventions

Active-high transparent



Active-low transparent




Positive (rising) edge



Negative (falling) edge



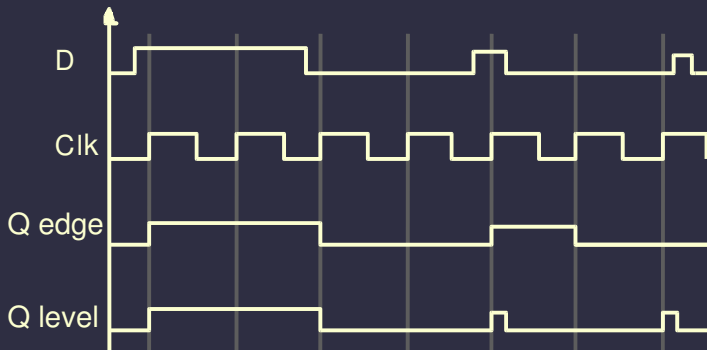
Timing for edge and level-sensitive latches




Falling edge-triggered D flip-flop

- Use two stages of latches
- When clock is high
 - First stage samples input w.o. changing second stage
 - Second stage holds value
- When clock goes low
 - First stage holds value and sets or resets second stage
 - Second stage transmits first stage
- $Q^+ = D$
- One of the most commonly used flip-flops

Falling edge-triggered D flip-flop

 


Falling edge-triggered D flip-flop

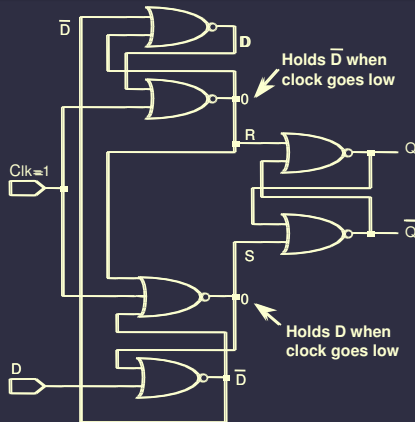

Clock switching

Inputs sampled on falling edge, outputs change after falling edge

Falling edge-triggered D flip-flop

 

Summary

- Memory
- Latches
- Flip-flops (more on these later)

Outline

1. Memory
2. Latches
3. Clocks
4. Homework

Reading assignment

- M. Morris Mano and Charles R. Kime. *Logic and Computer Design Fundamentals*. Prentice-Hall, NJ, fourth edition, 2008
- Sections 5.1–5.7
- Sections 6.1–6.4

Computer geek culture reference

Computer security

- PGP
- (Open)SSH
- (Type II) remailers
- Wireshark
- Crack