

Homework two

EECS 303: Advanced Digital Logic Design
Assigned 9 October 2008
Due 16 October 2008

You may discuss the assignment with your classmates.
However, you need to understand and write the solutions independently.

1. **(10 points)** Consider the following functions


$$f(a, b, c, d) = \bar{a}b\bar{c} + \bar{b}c + ac + \bar{a}\bar{b}c\bar{d}$$

$$g(a, b, c, d) = ab + \bar{a}bcd$$

$$h(a, b, c, d) = \bar{a}\bar{b}c\bar{d} + \bar{a}bcd$$

- (a) Draw a diagram for an implementation using a single PLA using a minimal number of AND gates. How many AND gates are required?
- (b) If you were to implement it with a PAL, how many AND gates would be required?
2. **(10 points)** Implement $f(a, b, c) = \sum(0, 3, 4) + d(2, 5, 7)$ using a $n : 1$ multiplexor where n is minimal. Draw the circuit diagram. What is n ?

 3. (10 points) Reimplement the following network using only NANDs and NORs. Assume there is no cost to invert inputs. You need not globally reorganize the network: local transformation is sufficient. Show a series of three or so circuit diagrams indicating your steps.



4. (5 points) Implement an exclusive or gate using steering logic. Assume access to complimented and uncomplimented input literals. Draw a diagram composed only of transmission gates. How many transmission gates are required?
5. (5 points) Implement an exclusive or using transmission gates. Assume access to complimented and uncomplimented input literals. Draw a diagram composed only of transmission gates. How many transmission gates are required?