

Advanced Digital Logic Design – EECS 303

<http://ziyang.eecs.northwestern.edu/eecs303/>

Teacher: Robert Dick
 Office: L477 Tech
 Email: dickrp@northwestern.edu
 Phone: 847-467-2298



**NORTHWESTERN
UNIVERSITY**

Sequential elements
Finite state machine design
Homework

Introduction
Reset/set latches
Clocking conventions
D flip-flop

Introduction to sequential elements


- Feedback and memory
- Memory
- Latches

Robert Dick Advanced Digital Logic Design

Sequential elements
Finite state machine design
Homework

Introduction
Reset/set latches
Clocking conventions
D flip-flop

TG and NOT-based memory

 


- Can break feedback path to load new value
- However, potential for timing problems

Robert Dick Advanced Digital Logic Design

Sequential elements
Finite state machine design
Homework

Introduction
Reset/set latches
Clocking conventions
D flip-flop

Reset/set timing

 

Robert Dick Advanced Digital Logic Design

Sequential elements
Finite state machine design
Homework

Introduction
Reset/set latches
Clocking conventions
D flip-flop

Flip-flop introduction


- Stores, and outputs, a value
- Puts a special clock signal in charge of timing
- Allows output to change in response to clock transition
- More on this later
 - Timing and sequential circuits

Robert Dick Advanced Digital Logic Design

Sequential elements
Finite state machine design
Homework

Introduction
Reset/set latches
Clocking conventions
D flip-flop

Feedback and memory

 


- Feedback is the root of memory
- Can compose a simple loop from NOT gates
- However, there is no way to switch the value

Robert Dick Advanced Digital Logic Design

Sequential elements
Finite state machine design
Homework

Introduction
Reset/set latches
Clocking conventions
D flip-flop

Reset/set latch

 


Robert Dick Advanced Digital Logic Design


Sequential elements
Finite state machine design
Homework

Introduction
Reset/set latches
Clocking conventions
D flip-flop



RS latch state diagram

 

 
Robert Dick Advanced Digital Logic Design



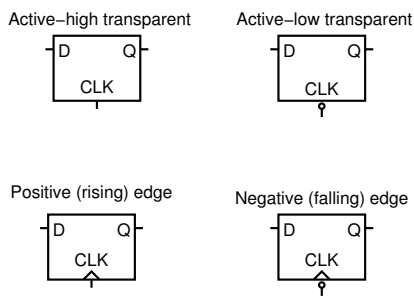 
- Clock – Rising edge, falling edge, high level, low level, period
- Setup time: Minimum time before clocking event by which input must be stable (T_{SU})
- Hold time: Minimum time after clocking event for which input must remain stable (T_H)
- Window: From setup time to hold time



 
- Minimum clock width, T_W
 - Usually period / 2
- Low to high propagation delay, P_{LH}
- High to low propagation delay, P_{HL}
- Worst-case and typical



Type	Inputs sampled	Outputs valid
Unclocked latch	Always	LFT
Level-sensitive latch	Clock high (T_{SU} to T_H) around falling clock edge	LFT
Edge-triggered flip-flop	Clock low-to-high transition (T_{SU} to T_H) around rising clock edge	Delay from rising edge

 

 Example, negative (falling) edge-triggered flip-flop timing diagram





- Minimum clock width, T_W
 - Usually period / 2
- Low to high propagation delay, P_{LH}
- High to low propagation delay, P_{HL}

S	R	Q^+	\bar{Q}^+	Notes
0	0	Q	\bar{Q}	
0	1	0	1	
1	0	1	0	
1	1	1	1	unstable



J	K	Q	Q^+	
0	0	0	0	hold
0	0	1	1	hold
0	1	0	0	reset
0	1	1	0	reset
1	0	0	1	set
1	0	1	1	set
1	1	0	1	toggle
1	1	1	0	toggle


- Use two stages of latches
- When clock is high
 - First stage samples input w.o. changing second stage
 - Second stage holds value
- When clock goes low
 - First stage holds value and sets or resets second stage
 - Second stage transmits first stage
- $Q^+ = D$
- One of the most commonly used flip-flops

  Example, positive (rising) edge-triggered flip-flop timing diagram




  Use output feedback to ensure that $RS \neq 11$
 $Q^+ = Q \bar{K} + \bar{Q} J$



 


 Clock switching
Inputs sampled on falling edge, outputs change after falling edge



- Versatile building block
- Building block for D and T flip-flops
- Has two inputs resulting in increased wiring complexity
- Don't use master/slave JK flip-flops
 - Ones or zeros catching
- Edge-triggered varieties exist

 - State changes each clock tick
- Useful for building counters
- Can be implemented with other flip-flops
 - JK with inputs high
 - D with XOR feedback



- Storage element in narrow width clocked systems
- Dangerous
- Fundamental building block of many flip-flop types

- Minimizes input wiring
- Simple to use
- Common choice for basic memory elements in sequential circuits

- How can a circuit with numerous distributed edge-triggered flip-flops be put into a known state
- Could devise some sequence of input events to bring the machine into a known state
 - Complicated
 - Slow
 - Not necessarily possible, given trap states
- Can also use sequential elements with additional asynchronous reset and/or set inputs

RS

$$Q^+ = S + \bar{R} Q$$


D

$$Q^+ = D$$

- We'll walk through the design of an example finite state machine (FSM)
- Some of the stages will be covered in more detail in later lectures
- I want you to have a high-level understanding of our overall goal before covering every detail of FSM synthesis

Can be expressed with regular expressions, examples

 - Accept the empty string, ϵ
- Accept nothing, \emptyset
- Accept 0 or 11, $(0 + 11)$
- Accept anything starting with 1 and one or more 0 and ending with 0 or 10, $10^+(0 + 10)$
- Accept anything starting with zero or more 0010 or 1 and ending with 1, $(0010 + 1)^*1$



JK

$$Q^+ = J \bar{Q} + \bar{K} Q$$

T


$$Q^+ = T \oplus Q$$

- Naturally express control
- However, no simple direct HW implementation
- We want to get to sequential logic
- Need to go through other stages first

- State graph
- Multiple states can be active at the same time
- Some states ACCEPT
- The automata accepts if any accepting states are active

- NFAs require multiple states to be simultaneously active
- Can't represent this with conventional logic state variables
- Need to convert to deterministic representation


DFA

 

DFA to FSM

- DFA may only accept or reject
- Simple to convert Moore FSM
- Add explicit output values to states


Mealy block diagram

 


Introduction to state reduction

s	s ⁺		Q
	0	1	
A	A	B	0
B	C	B	0
C	A	B	0
D	A	A	1


DFA to more explicit FSM

 

Moore block diagram

 

Moore FSMs

 

Introduction to state reduction


s	s ⁺		q
	0	1	
AC	AC	B	0
B	AC	B	0
D	AC	AC	1

	s ⁺			
s	0	1	q	
ABC	ABC	ABC	0	
D	ABC	ABC	1	



Only two adjacent states, state assignment is trivial
However, good to consider output, q

	s ⁺			
s	0	1	q	
0	0	0	0	
1	0	0	1	

s⁺(s) = 0
q(s) = s

 

	s ⁺ /q	
s	0	1
A	D/0	B/X
B	C/1	B/0
C	A/0	B/1
D	C/1	C/0

  

- Separate sequential and combinational portions of circuit
- Conduct standard logic synthesis

- Specify requirements in natural form – regular expression or NFA
- Converting from NFA to DFA is straightforward
- Converting from DFA to FSM is straightforward
- Minimize the number of states using compatible states, class sets, and binate covering
- Assign values to states to minimize logic complexity
- Allow only adjacent or path transitions for asynchronous machines
- Optimize implementation of state and output functions

- M. Morris Mano and Charles R. Kime. *Logic and Computer Design Fundamentals*. Prentice-Hall, NJ, third edition, 2004
- Chapter 7
- Chapter 6

Video controller repair lab

- Design a finite state machine based on an English problem specification
- The design problem isn't very difficult
- Going from a real-world problem to a formal representation may be difficult
- Be careful not to use too many state variables!!!
 - Could easily turn it from a 6-hour lab to a 12-hour lab

Next lecture

- More detail and examples on FSM design and optimization