

# EECS 312 Discussion 13

## Review 2

12/03

Shengshuo Lu  
(luss@umich.edu)

# Logic Effort

# Logical Effort Motivation

- Sizing of a chain of inverters
  - Geometric progression
- How about more complex logic?
- Logical Effort objectives:
  - Quick & dirty, back of the envelope sizing
  - Make trade-off between circuits
  - What is the best circuit topology for a function?
  - How many stages of logic give least delay?
  - How wide should the transistors be?

# Delay in a Logic Gate


- Express delays in process-independent unit
- Delay has two components:

$$d = f + p$$


- *f*: effort delay =  $gh$  (a.k.a. stage effort)
  - Again has two components
- *g*: logical effort
  - Measures relative ability of gate to deliver current
  - $g \equiv 1$  for inverter
- *h*: electrical effort =  $C_{\text{out}} / C_{\text{in}}$ 
  - Ratio of output to input capacitance
  - Sometimes called fanout
- *p*: parasitic delay
  - Represents delay of gate driving no load
  - Set by internal parasitic capacitance
 
# Computing Logical Effort


- DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current (i.e, effort delay under same loading).*
- Measure from delay vs. fanout plots
- Or estimate by counting transistor widths



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$


# Logical effort (g)

Number of inputs


Gate type	1	2	3	4	5	n
Inverter	1					
NAND		$4/3$	$5/3$	$6/3$	$7/3$	$(n + 2)/3$
NOR		$5/3$	$7/3$	$9/3$	$11/3$	$(2n + 1)/3$
Multiplexer		2	2	2	2	2
 
# Computing Parasitic Delay


- Measure from delay vs. fanout plots
- Or estimate by counting self loading on output node for sizing with equal output current to inverter
- For simplification, we ignore internal node capacitance



$$C_{out} = 3$$
$$p = 3/3$$

 

$$C_{out} = 6$$
$$p = 6/3 = 2$$

 


$$C_{out} = 6$$
$$p = 6/3 = 2$$

# Parasitic Delay ( $p$ )


Gate type	Parasitic Delay
Inverter	$p_{inv}$
n-input NAND	$n \cdot p_{inv}$
n-input NOR	$n \cdot p_{inv}$
n-way multiplexer	$2n \cdot p_{inv}$



# Delay components

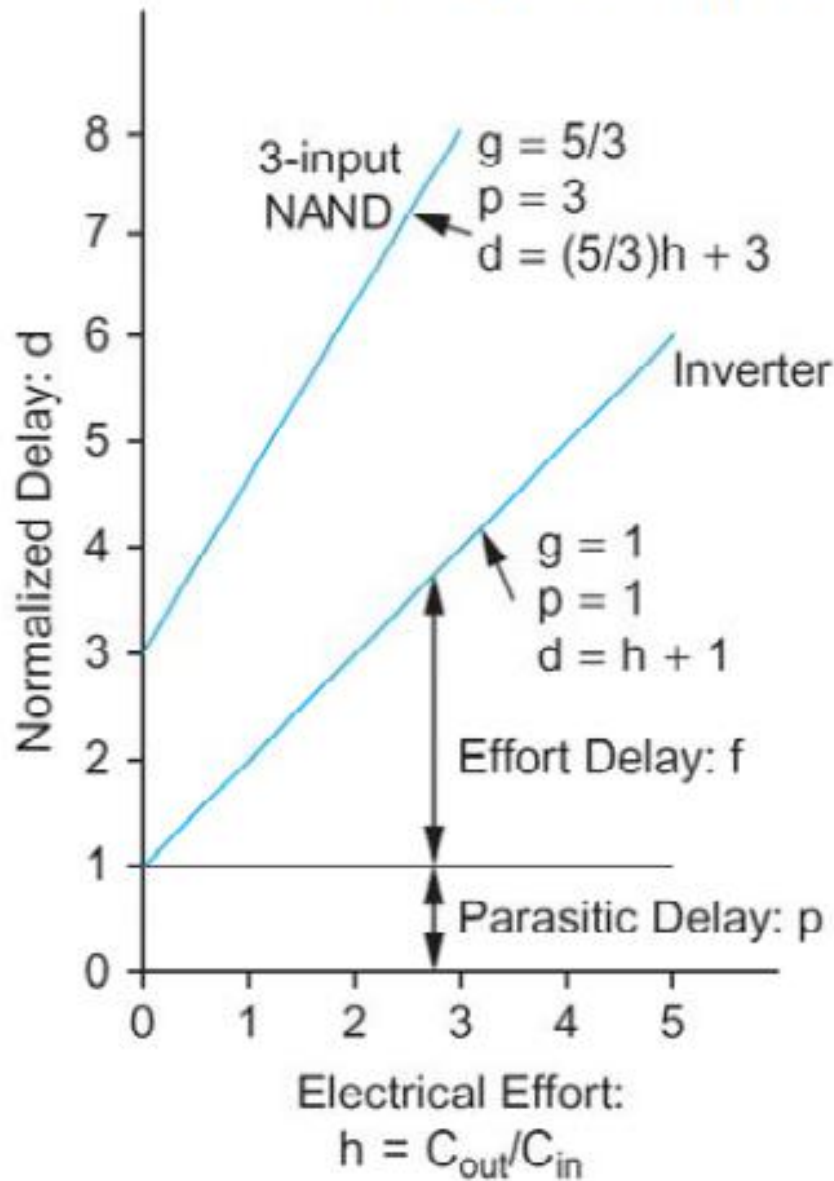

# Fanout 4 Example

 

$$C_{out} = 4C_{in}$$

$$h = 4$$

$$g = 1$$

$$p = 1$$

$$D = 4 + 1 = 5\tau$$

FO4 delay

96ps of 250nm


# Logic Effort

- Uncovered Topic: Branch

# Static Logic Families

 
# Classic CMOS

- Advantages:
  - Non-ratioed
  - $\sim 0$  static power
  - Low S.C. power  $\sim 10\%$  of dynamic power
  - Full rail swing
  - Good noise margins
  - True and complement functions



 
# Classic CMOS


- Disadvantages:
  - Large # of transistors, large area
  - Slow
    - PMOS mobility
    - Transistor cap from dual function
  - Increasing static power due to leakage



Tradeoff

 

 
# Differential Cascode Voltage Switch DCVS




PMOS stack with NMOS
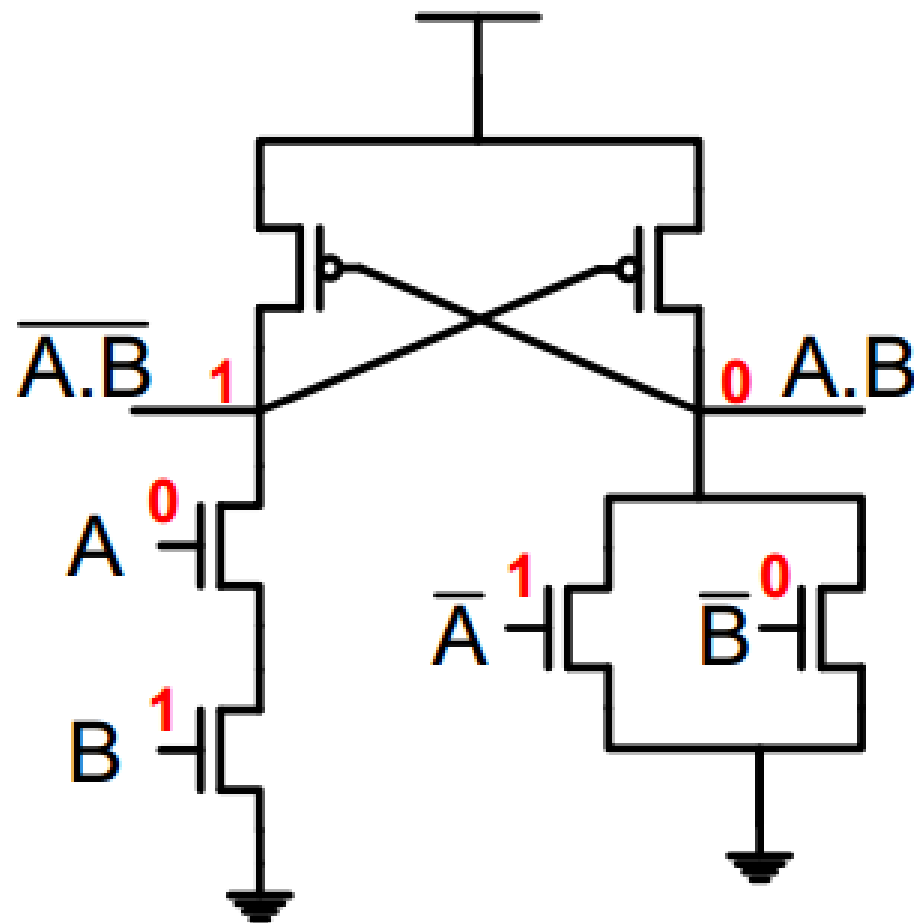
# Differential Cascode Voltage Switch DCVS






 
# Differential Cascode Voltage Switch DCVS


 
# Differential Cascode Voltage Switch DCVS



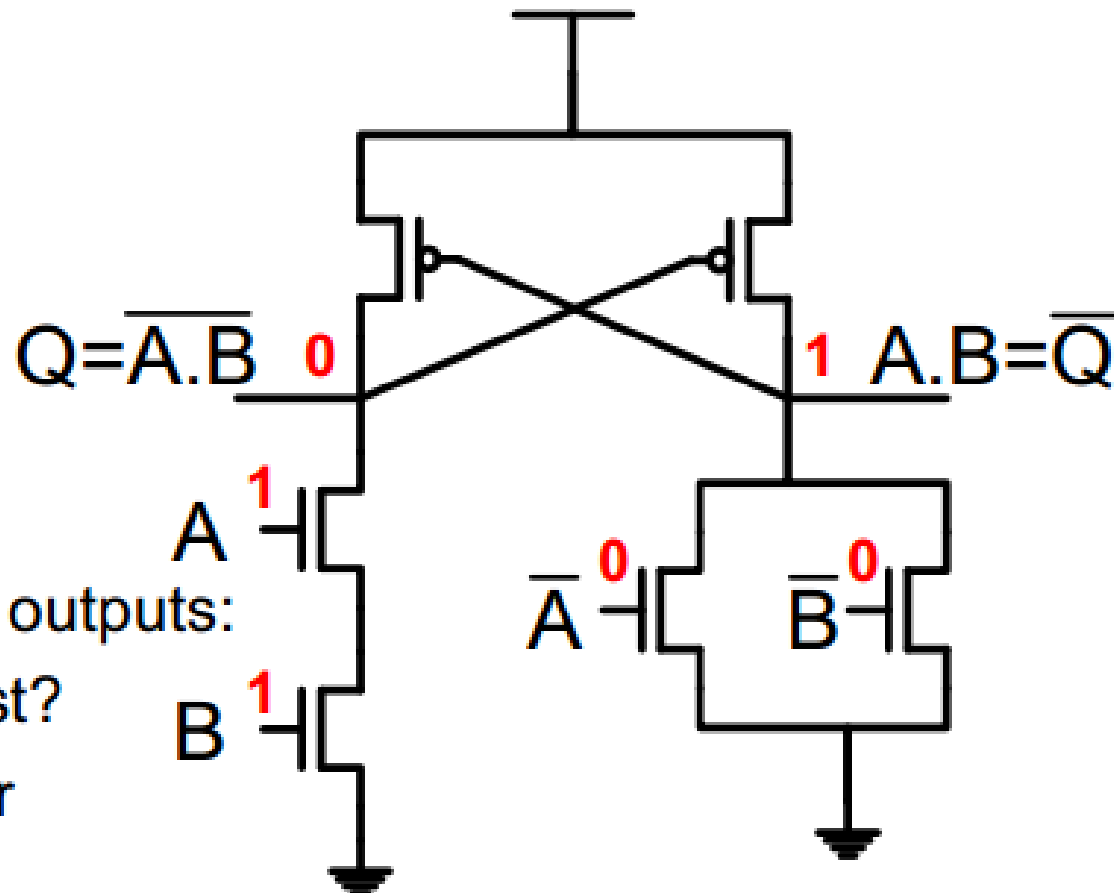
# Differential Cascode Voltage Switch DCVS




Timing of outputs:  
Which first?  
Q or Qbar
 
# Differential Cascode Voltage Switch DCVS




- Advantages:
  - No PMOS duality
    - Lower input cap.
    - Use only NMOS
  - Faster than CMOS
  - Can evaluate complex logic trees in 1 stage
 
# Differential Cascode Voltage Switch DCVS




- Disadvantages:
  - Need complementary inputs (dual rail)
  - Cross-bar current
    - Sensitive to input timing
  - Sizing of PMOS is hard
    - Too large  $\rightarrow$  PDN does not switch the output
    - Too small  $\rightarrow$  Slow rise time
- Ratioed Logic?

# Pass Gate Logic

 


- **Advantages:**
  - Speed: 20-50% faster (less capacitance)
    - In some circuits, such as XOR/MUX
  - Lower dynamic power

# Pass Gate Logic

 

- Disadvantages:
  - Very sensitive to noise: 2 types
    - $V_t$  drop  $\rightarrow$  must level restore someplace
    - Sensitive to undershoot voltage noise on inputs
      - Buffers at inputs suppresses this effect
  - Body effect  $\rightarrow$  limit # of FETs in series

# Pass Gate Logic

 


- **Disadvantages:**

- Delay dependence on state
- Cannot be cascaded without output inverter
- Added leakage in output inverter



# Dynamic Logic Families


# Basic Domino gate

 


- Divide the clock in 2 phases:
  - Precharge
    - Output Low
    - Dyn. Cap precharge
    - PDN Off
  - Evaluate
    - Conditional discharge
    - Input must be stable and monotonic L→H

# Domino / Static $C_{in}/C_{out}$

3-input OR gate

 


Static:  
 $C_i = 7$   
 $C_n = 9$

 

Dynamic:  
 $C_i = 2$   
 $C_n = 7$


# Basic Domino gate

 

## • Advantages:

- Faster than CMOS
- Input capacitance is lower
- Early switch point
- Inverter  $P/N > 2$  (only rising delay important)


# Basic Domino gate

 

## Disadvantages:


- Low noise margin
- Charge sharing
- Leakage currents
- Internal capacitance charge sensitive to noise

# Issues: Leakage

 

- Dynamic node is floating during evaluation
  - Leakage current of NMOS can discharge it


# Issues: Leakage

 

- Half latch devices:
  - Size PMOS to replenish the leakage current
  - Limits width OR gates



# Domino – with and without keeper

Graph0

 





# Issues: Charge sharing

  


- In evaluate, dynamic node charge is shared with internal node caps
- Node was discharged in previous cycle

# Sequential Logic

# Flip-flop (Basics)

  

# Flip-flop


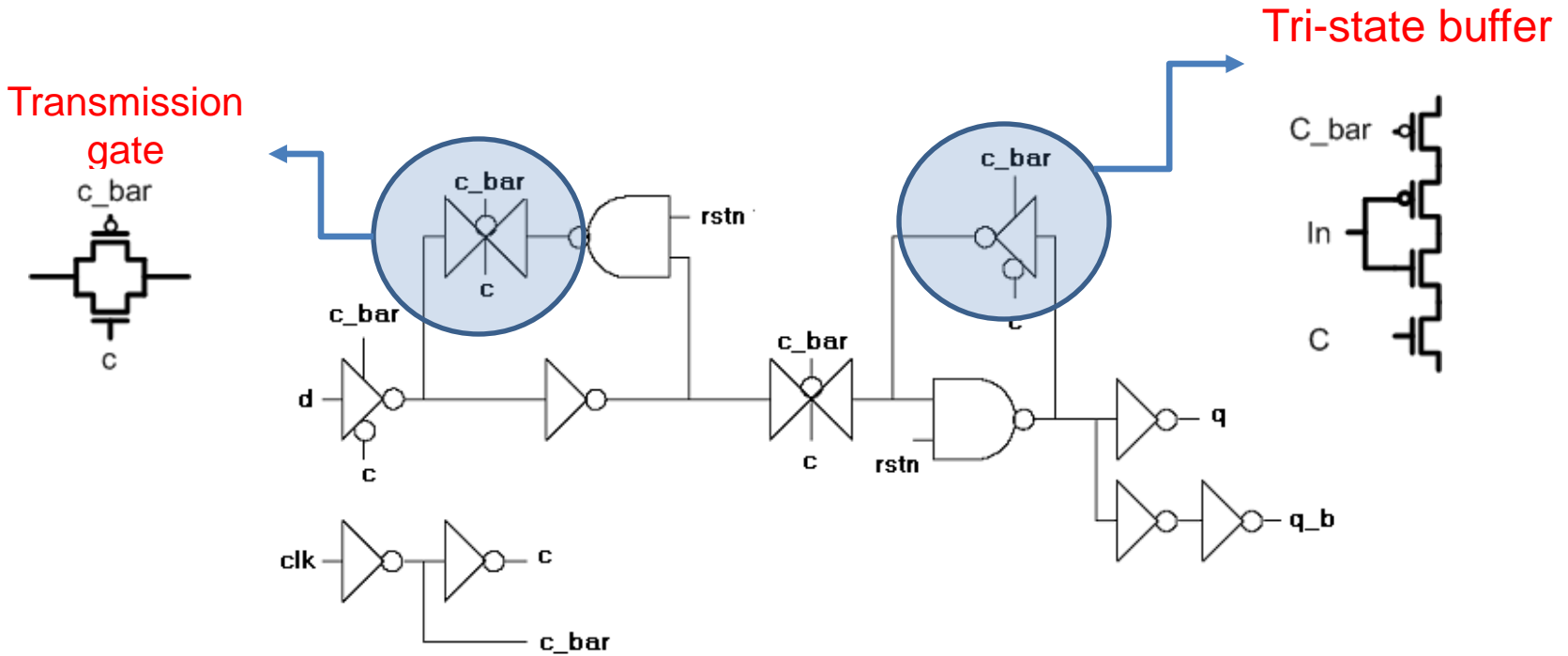


- Flip Flop with Asynchronous Reset

# Flip-flop

 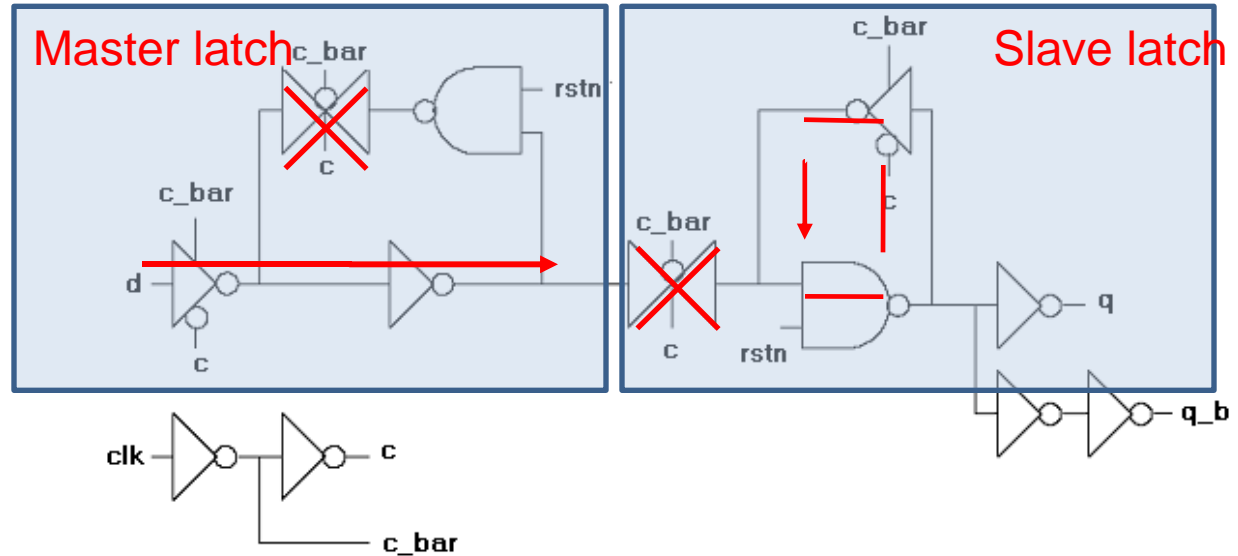
## How it works

- Divided flip flop into 2 latches (master and slave)
- When master is transparent, slave holds.
- When master holds, slave is transparent
- Capture data at the rising edge of clock



# Flip-flop (continued)


- Important terms : C-Q delay, D-Q delay

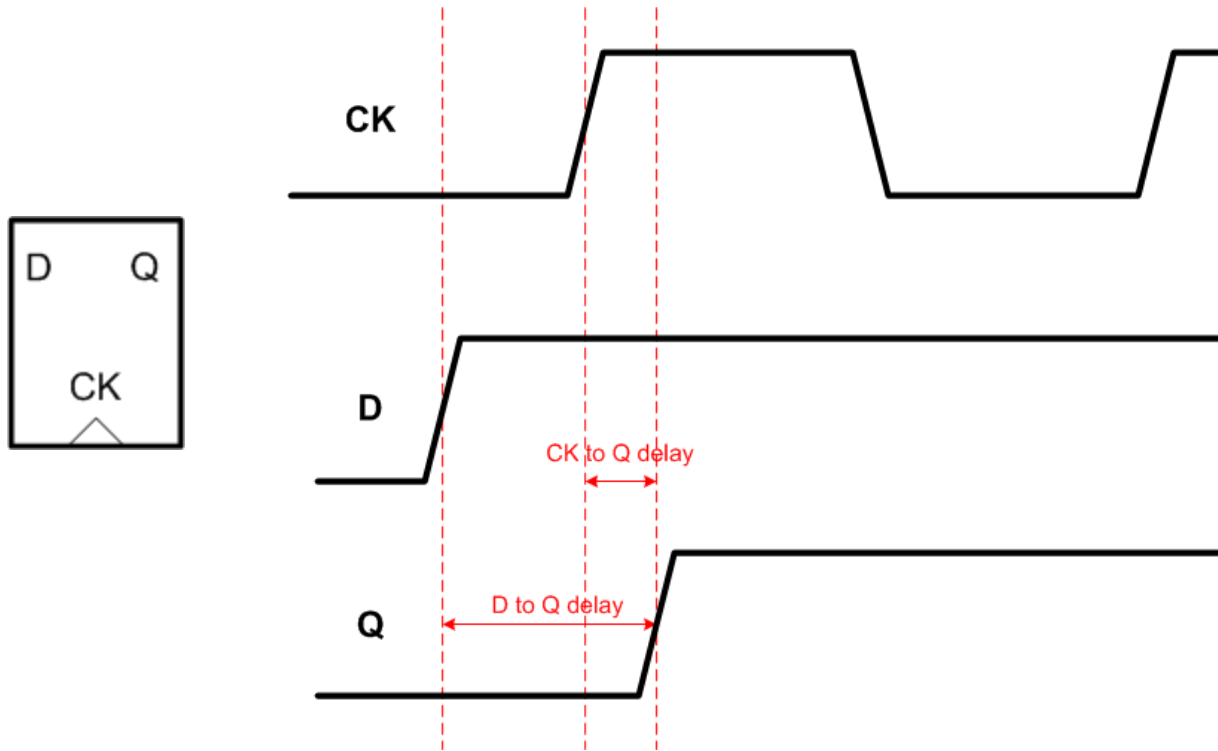
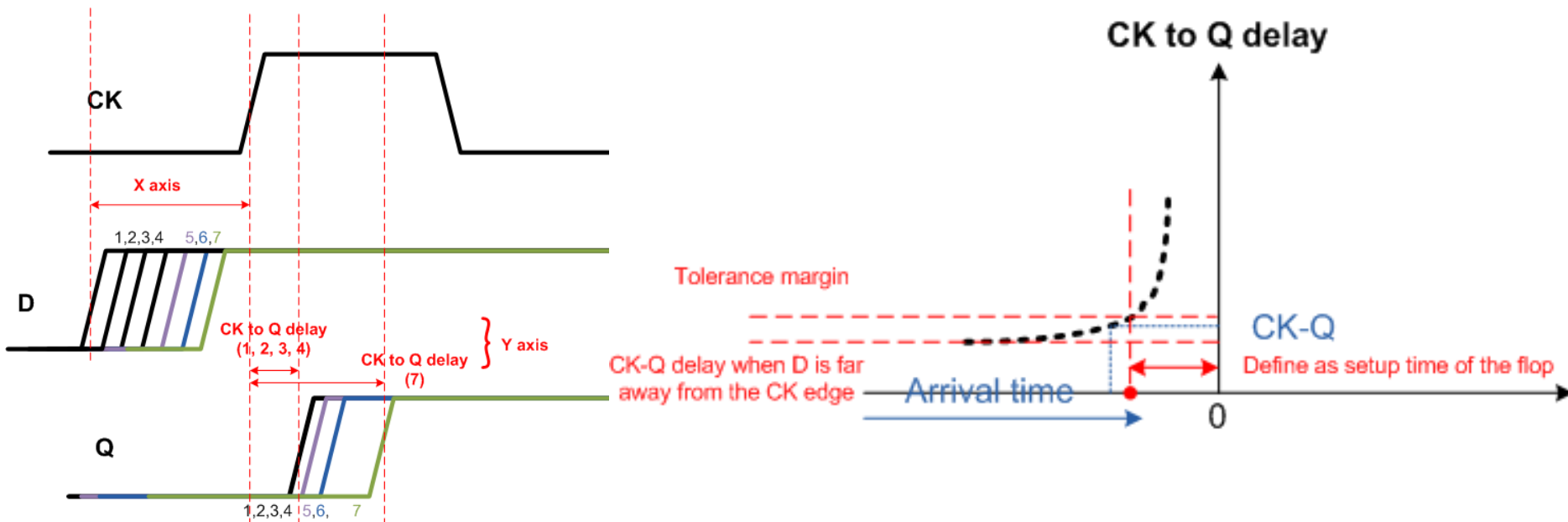
# Flip-flop (continued)

- Setup Time

- As D approaches to CK edge, C-Q delay goes up





When D arrives after the setup time point, we call it setup time violation

Setup-Time : Point at which CLK-Q delay rises 5% beyond nominal
  
# Flip-flop (continued)


- Hold Time

- Input should be stable for a period of time after the clk edge







# Synchronous Timing

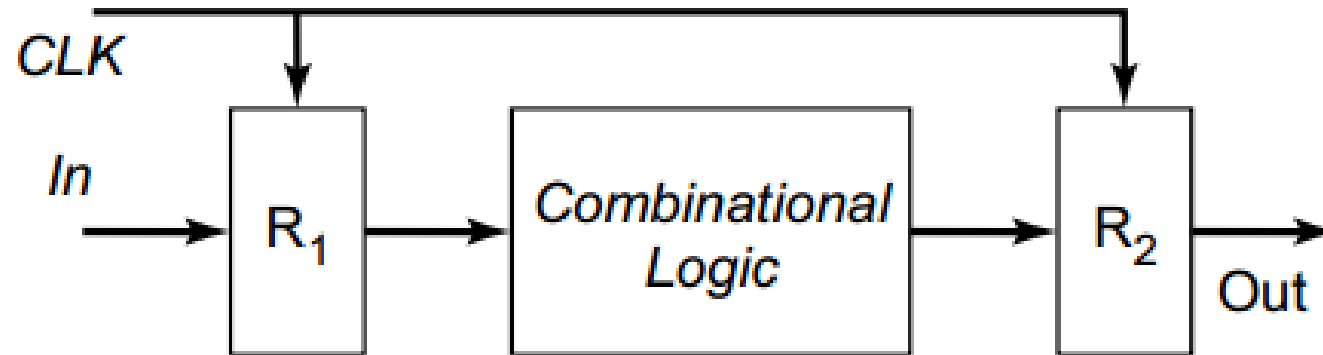

# Timing Metrics

 

# Synchronous Timing

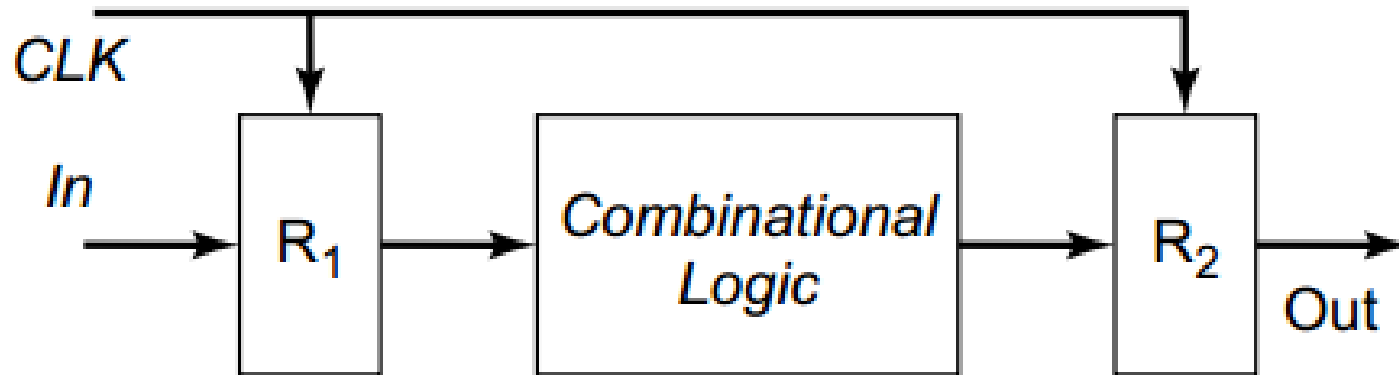

$$T_{c-q} + t_{plogic,min} \geq t_{hold}$$

$$T \geq t_{c-q} + t_{plogic,max} + t_{su}$$

# SRAM & DRAM

- Office Hour

# Review 1

- MOSFET Transistor
- CMOS Gate
- Power
- Diode Behavior and equation
- Transistor Behavior and equation
- RC Delay
- Capacitance
- Size Single Gate

# Review 2

- Logic Effort
- Static Logic Family
- Dynamic Logic Family
- Sequential Logic
- Synchronous Timing
- SRAM & DRAM