
 
 


# Digital Integrated Circuits – EECS 312

<http://robertdick.org/eecs312/>

Teacher: Robert Dick  
Office: 2417-E EECS  
Email: dickrp@umich.edu  
Phone: 734-763-3329  
Cellphone: 847-530-1824

 GSI: Shengshou Lu  
Office: 2725 BBB  
Email: luss@umich.edu



# Lecture plan


1. Lab one
2. Desired transistor behavior
3. Homework

# Lab one challenges

- Learning to use the tools (last Friday).
- Understanding the circuits used in the lab (today).
- A note on the CAD tools market.

Derive and explain.

# NMOS inverter schematic

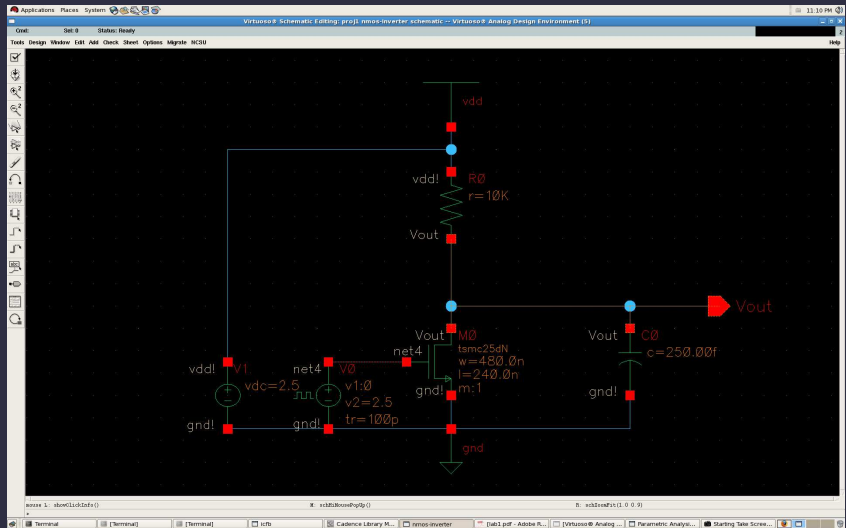

# Resistance

$$R = \rho \frac{L}{W} \quad (1)$$


$$G = \sigma \frac{W}{L} \quad (2)$$

$$G = \frac{1}{R} \quad (3)$$

$$\sigma = \frac{1}{\rho} \quad (4)$$

- Assuming fixed height.
- $R$ : resistance.
- $\rho$ : resistivity.
- $L$ : length.
- $W$ : width.
- $G$ : conductance.

# NMOS inverter simulation results

 

# RC network



$$V_c = V_{final} + (V_{init} - V_{final}) e^{\frac{-t}{\tau}} \quad (5)$$

$$\tau = RC \quad (6)$$

# NMOS→CMOS inverter

- How does structure change?
- What impact does transistor width have? Why different widths?
- How does response change?
- What are advantages?
- What are disadvantages?

Derive and explain.



## Review questions and note

- What are digital systems built from?
- What gate properties are required for use in digital systems? Why?
- What have the major effects of process scaling been? What challenges does it face in the future?
- What are the physical structures and symbols of (N/P)MOSFETs? How do they work?

# Lecture plan

1. Lab one
2. Desired transistor behavior
3. Homework

# Desired and actual properties of transistors

## Desired properties

- Perfect digital signal transfer.
- No parasitics.

## Actual properties

- Imperfect transfer function.
  - Fortunately, has gain and capable of signal regeneration (restoration).
- Parasitic resistance and capacitance.
- Leakage.

# Brief introduction to Boolean algebra

- The only values are 0 (or false) and 1 (or true).
- One can define operations/functions/gates.
  - Boolean values as input and output.
- A truth table enumerates output values for all input value combinations.

# AND

a	b	$a \wedge b$
0	0	0
0	1	0
1	0	0
1	1	1



$$a \text{ AND } b = a \wedge b = a b$$

# OR

a	b	a + b
0	0	0
0	1	1
1	0	1
1	1	1



$$a \text{ OR } b = a \vee b = a + b$$


# NOT

a	$\bar{a}$
0	1
1	0




$$\text{NOT } a = \bar{a}$$

# CMOS inverter operation

 





# CMOS inverter operation

 


# CMOS inverter operation

 


# CMOS inverter operation

 


# CMOS inverter operation

 


# CMOS inverter operation

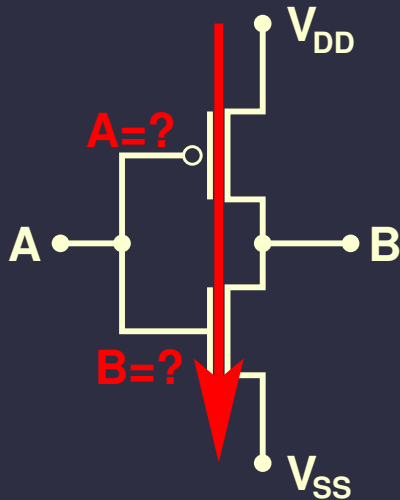


# NAND operation

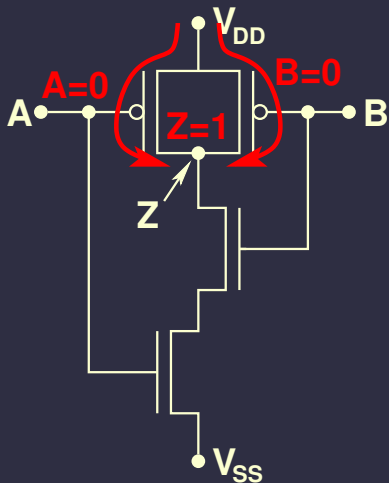

# NAND operation

 


# NAND operation

 





# NAND operation

 


# NAND operation

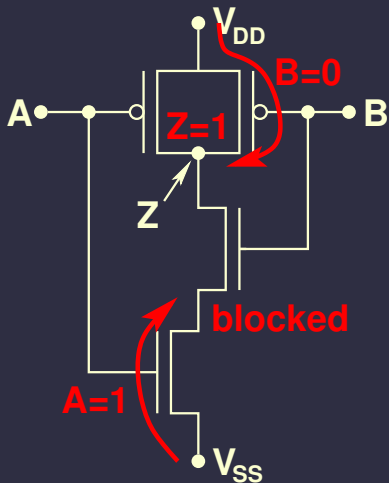


# NAND operation

 

# NAND operation

 


# NAND operation

 

 
# NAND gate

- Therefore, *NAND* and *NOR* gates are used in CMOS design instead of *AND* and *OR* gates



 
# NAND gate

- Therefore, *NAND* and *NOR* gates are used in CMOS design instead of *AND* and *OR* gates




# NAND layout

 





# NOR operation

 


# NOR operation

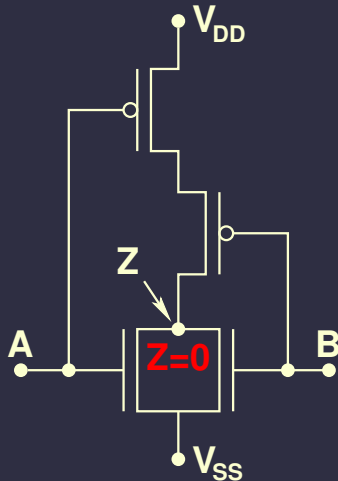


# NOR operation

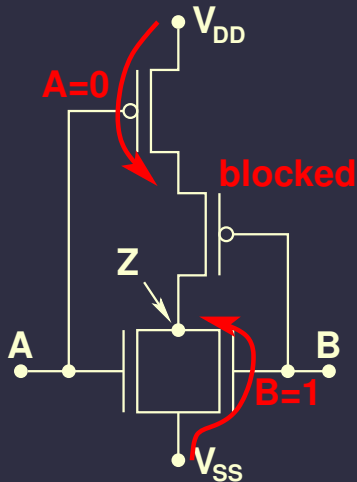


# NOR operation

 


# NOR operation

 

# NOR operation

 

# NOR operation

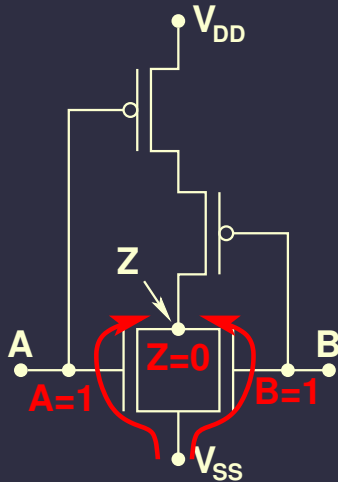


# CMOS transmission gates (switches)


- NMOS is good at transmitting 0s
  - Bad at transmitting 1s
- PMOS is good at transmitting 1s
  - Bad at transmitting 0s
- To build a switch, use both: CMOS




# CMOS transmission gate (TG)

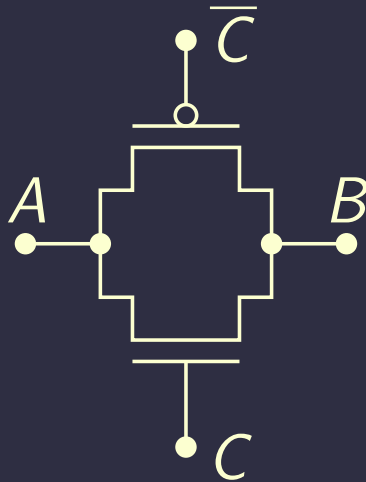


# CMOS transmission gate (TG)

 


# CMOS transmission gate (TG)

 


# CMOS transmission gate (TG)

 


# CMOS transmission gate (TG)

 


# CMOS transmission gate (TG)

 

# CMOS transmission gate (TG)

 


# CMOS transmission gate (TG)


 




# CMOS transmission gate (TG)

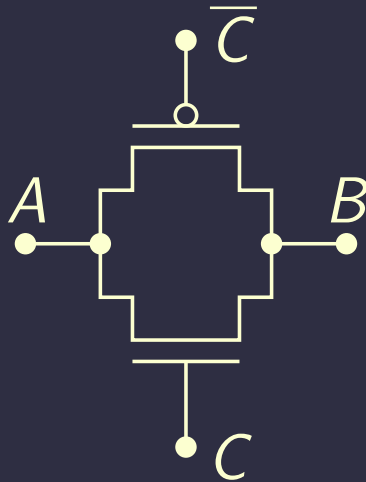

# Other TG diagram

  

## Logic gates vs. TGs

- What can each be used to implement?
- How to decide which to use?

# Upcoming topics

- Diodes.
- Transistor static behavior.
- Transistor dynamic behavior.

# Lecture plan

1. Lab one
2. Desired transistor behavior
3. Homework

# Homework assignment and announcement

- 12 September: Read Section 3.3.2 in J. Rabaey, A. Chandrakasan, and B. Nikolic. *Digital Integrated Circuits: A Design Perspective*. Prentice-Hall, second edition, 2003.
- 17 September: Laboratory assignment one.