 


3. (10 pts.) Show the side view of the basic memory element used in an EPROM. Using at most two sentences, explain the process of programming it. Using at most two sentences, explain the process of erasing it.

4. (10 pts.) What does this layout show? What is its greatest performance irregularity or flaw? In other words, if you were to implement the same function, how would your solution differ? Use at most four sentences.



5. **(10 pts.)** List one problem caused by hot carriers and one profitable use of them. Use at most four sentences.

6. **(5 pts.)** What controls whether carbon nanotubes are metallic or semi-conducting? Use at most one sentence.

2 Analysis and Design

7. **(10 pts.)** You designed a CMOS inverter to have a $V_M = V_{DD}/2$. However, its fabrication was not perfect. Impurities mixed in with the acceptor ions introduced strain in the NMOSFET, increasing its carrier mobility by 50%. What is the impact on V_M ?

8. **(10 pts.)** Generalize the concept of carry-select addition to multiplication. Show the diagram of a carry-select combinational multiplier for two 3-bit numbers. Indicate the impact on performance, assuming that the MUX overhead is negligible. You may use boxes labeled HA, FA, and MUX without showing their transistor-level designs.

9. **(15 pts.)** Draw a diagram of an SRAM with 16 addresses, each of which stores one bit. Take your design down to transistor level, but use hierarchy. Focus on correctness, not efficiency for this question. Your inputs are the four address lines. Implementing the read functionality is sufficient.

10. **(15 pts.)** Determine the period of oscillation for a ring of three balanced inverters with minimal-width NMOSFETs. Explicitly state any simplifying assumptions you make. The diffusion region lengths are all $0.5\ \mu\text{m}$, but don't assume that my stating this requires that you use it.

Question 10 was the last question. You are done. Have a good break.

3 Reference material

	C_{OX} (fF/ μm^2)	C_O (fF/ μm)	C_j (fF/ μm^2)	m_j	ϕ_b (V)	C_{jsw} (fF/ μm)	m_{jsw}	ϕ_{bsw} (V)
NMOS	6	0.31	2	0.5	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9

MODELS FOR CMOS DEVICES

CMOS (0.25 μm) – Unified Model.

	V_{T0} (V)	γ (V ^{0.5})	V_{DSAT} (V)	k' (A/V ²)	λ (V ⁻¹)
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

CMOS (0.25 μm) – Switch Model (R_{eq})

V_{DD} (V)	1	1.5	2	2.5
NMOS (k Ω)	35	19	15	13
PMOS (k Ω)	115	55	38	31

CMOS (0.25 μm) – BSIM Model

See Website: <http://bwrc.eecs.berkeley.edu/IcBook>

Name	Value
kT/q	25.875 mJ/C
NMOSFET I_S	21.0 pA
PMOSFET I_S	41.8 pA
n (for I_D calculation)	1.5

$$V_M = \frac{\left(V_{Tn} + \frac{V_{DSATn}}{2}\right) + r \left(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2}\right)}{1 + r}$$

$$r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{\nu_{satp} W_p}{\nu_{satn} W_n}$$

VALUES OF MATERIAL AND PHYSICAL CONSTANTS

Name	Symbol	Value	Units
Room temperature	T	300 (= 27°C)	K
Boltzman constant	k	1.38×10^{-23}	J/K
Electron charge	q	1.6×10^{-19}	C
Thermal voltage	$\phi_T = kT/q$	26	mV (at 300 K)
Intrinsic Carrier Concentration (Silicon)	n_i	1.5×10^{10}	cm^{-3} (at 300 K)
Permittivity of Si	ϵ_{si}	1.05×10^{-12}	F/cm
Permittivity of SiO ₂	ϵ_{sio_2}	3.5×10^{-13}	F/cm
Resistivity of Al	ρ_{Al}	2.7×10^{-8}	$\Omega\text{-m}$
Resistivity of Cu	ρ_{Cu}	1.7×10^{-8}	$\Omega\text{-m}$
Magnetic permeability of vacuum (similar for SiO ₂)	μ_0	12.6×10^{-7}	Wb/Am
Speed of light (in vacuum)	c_0	30	cm/nsec
Speed of light (in SiO ₂)	c_{sio_2}	15	cm/nsec

Definitions useful in gate sizing

g_i	Gate logical effort. Ratio of input capacitor to equal on-resistance inverter.
$G = \prod_{i=1}^n g_i$	Path logical effort.
$H = \frac{C_{out}}{C_{in}}$	Path electrical effort.
$b = \frac{C_{total}}{C_{useful}}$	Stage branching effort.
$B = \prod_{i=1}^n b_i$	path branching effort.
$F = GBH$	path effort.
$\hat{f} = g_i h_i = \sqrt[n]{F}$	Optimal stage effort.
$\hat{h}_i = \frac{\hat{f}}{g_i} = \frac{C_{i,out}}{C_{i,in}}$	Optimal stage electrical effort.
$D_i = G_i h_i + p_i$	Stage delay.

For sizing inverters, $\forall_{i=1}^n b = g = 1$.

FORMULAS AND EQUATIONS

Diode

$$I_D = I_S(e^{V_D/\phi_T} - 1) = Q_D/\tau_T$$

$$C_j = \frac{C_{j0}}{(1 - V_D/\phi_0)^m}$$

$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1 - m)} \times [(\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m}]$$

MOS Transistor

$$V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$$

$$I_D = \frac{k'_n W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \text{ (sat)}$$

$$I_D = v_{sat} C_{ox} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right) (1 + \lambda V_{DS}) \text{ (velocity sat)}$$

$$I_D = k'_n \frac{W}{L} \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right) \text{ (triode)}$$

$$I_D = I_S e^{\frac{V_{GS}}{n k T / q}} \left(1 - e^{-\frac{V_{DS}}{k T / q}} \right) \text{ (subthreshold)}$$

Deep Submicron MOS Unified Model

$$I_D = 0 \text{ for } V_{GT} \leq 0$$

$$I_D = k' \frac{W}{L} \left(V_{GT} V_{min} - \frac{V_{min}^2}{2} \right) (1 + \lambda V_{DS}) \text{ for } V_{GT} \geq 0$$

with $V_{min} = \min(V_{GT}, V_{DS}, V_{DSAT})$
and $V_{GT} = V_{GS} - V_T$

MOS Switch Model

$$R_{eq} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right)$$

$$\approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD} \right)$$

Inverter

$$V_{OH} = f(V_{OL})$$

$$V_{OL} = f(V_{OH})$$

$$V_M = f(V_M)$$

$$t_p = 0.69 R_{eq} C_L = \frac{C_L (V_{swing}/2)}{I_{avg}}$$

$$P_{dyn} = C_L V_{DD} V_{swing} f$$

$$P_{stat} = V_{DD} I_{DD}$$

Static CMOS Inverter

$$V_{OH} = V_{DD}$$

$$V_{OL} = GND$$

$$V_M \approx \frac{r V_{DD}}{1 + r} \text{ with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

with $g \approx \frac{1 + r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 0.69 C_L \left(\frac{R_{eqn} + R_{eqp}}{2} \right)$$

$$P_{av} = C_L V_{DD}^2 f$$

Interconnect

Lumped RC: $t_p = 0.69 RC$

Distributed RC: $t_p = 0.38 RC$

RC-chain:

$$\tau_N = \sum_{i=1}^N R_i \sum_{j=i}^N C_j = \sum_{i=1}^N C_i \sum_{j=1}^i R_j$$

Transmission line reflection:

$$\rho = \frac{V_{refl}}{V_{inc}} = \frac{I_{refl}}{I_{inc}} = \frac{R - Z_0}{R + Z_0}$$

CMOS COMBINATIONAL LOGIC

Transistor Sizing using Logical Effort

$$F = \frac{C_L}{C_{g1}} = \prod_1^N \frac{f_i}{b_i} \quad G = \prod_1^N g_i \quad D = t_{p0} \sum_{j=1}^N \left(p_j + \frac{f_j g_j}{\gamma} \right)$$

$$B = \prod_1^N b_i \quad H = FGB \quad D_{min} = t_{p0} \left(\sum_{j=1}^N p_j + \frac{N(\sqrt[N]{H})}{\gamma} \right)$$