

EECS 312: Digital Integrated Circuits  
Midterm Exam

12 March 2009

Robert Dick

Show your work. Derivations are required for credit; end results are insufficient.  
Closed book. No electronic mental aids.

Honor Pledge: I have neither given nor received aid in this exam.

Signature:


1. **(5 pts.)**  $k_n = \frac{W\mu_n\epsilon_{ox}}{Lt_{ox}}$  When the move from SiO<sub>2</sub> to high- $\kappa$  gate dielectric occurred, what qualitative changes were made to the variables upon which  $k_n$  depends? Use only a few sentence fragments for your answer.
2. **(10 pts.)** Consider a static CMOS gate implementing the following function:

$$f(a, b, c) = ab + \bar{b}c$$

This gate is subjected to the following transition  $a = 1, b = 0, c = 1 \rightarrow a = 1, b = 1, c = 1$ . Will the gate's dynamic energy consumption be greater if its inputs come from other static CMOS gates and inverters, or from DCVSL gates? Use one sentence to explain why. You may also use a schematic if that makes your answer clearer.

3. **(10 pts.)** Given process variation resulting in a Gaussian distribution of threshold voltage around its nominal value, will total integrated circuit sub-threshold leakage power consumption be higher, the same, or lower than that of an integrated circuit in which all transistors have nominal threshold voltages? Use at most two sentences to explain why.
4. **(10 pts.)** Determine the high-to-low propagation delay for an inverter with a 500 nm wide NMOSFET and a 1  $\mu$ m wide PMOSFET with its output connected to another identical inverter. Assume the default 250 nm process. Do consider overlap capacitance. Recall that it is necessary to consider both bottom and sidewall capacitance. You may neglect the resistance and capacitance of the wire connecting the two inverters. Note that the switch model reference table gives values for  $W/L =$  transistors. Show your work.
5. **(10 pts.)** Assuming the default 250 nm process, determine the minimum and maximum percentage change in subthreshold leakage current of a minimal-width NMOSFET given that the threshold voltage may deviate by 0.1 V from the nominal in either direction. You may assume that  $n = 1.5$ .

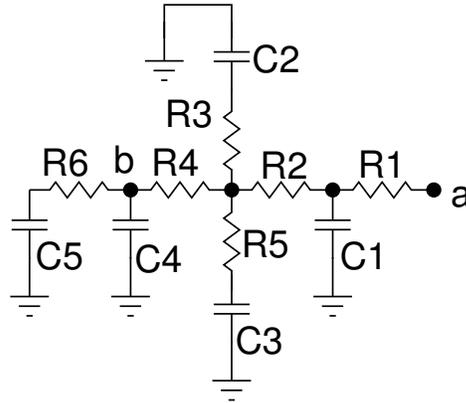6. (10 pts.) Determine the Elmore delay from Node a to Node b in the following circuit.




7. (10 pts.) Show the circuit diagram for a static CMOS implementation of the following function sized to have the same resistance to ground and  $V_{DD}$  as an inverter with a  $W$  wide NMOSFET and an  $2W$  wide PMOSFET. You may assume access to complemented and uncomplemented input literals, i.e.,  $a$  and  $\bar{a}$ .

$$f(a, b, c) = (ab + \bar{a}\bar{b})c$$

8. (0 pts.) Was this exam  tricky and surprising or did it  fairly closely follow the material we focused on in class?

	$C_{OX}$ (fF/ $\mu\text{m}^2$ )	$C_O$ (fF/ $\mu\text{m}$ )	$C_j$ (fF/ $\mu\text{m}^2$ )	$m_j$	$\phi_b$ (V)	$C_{jsw}$ (fF/ $\mu\text{m}$ )	$m_{jsw}$	$\phi_{bsw}$ (V)
NMOS	6	0.31	2	0.5	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9

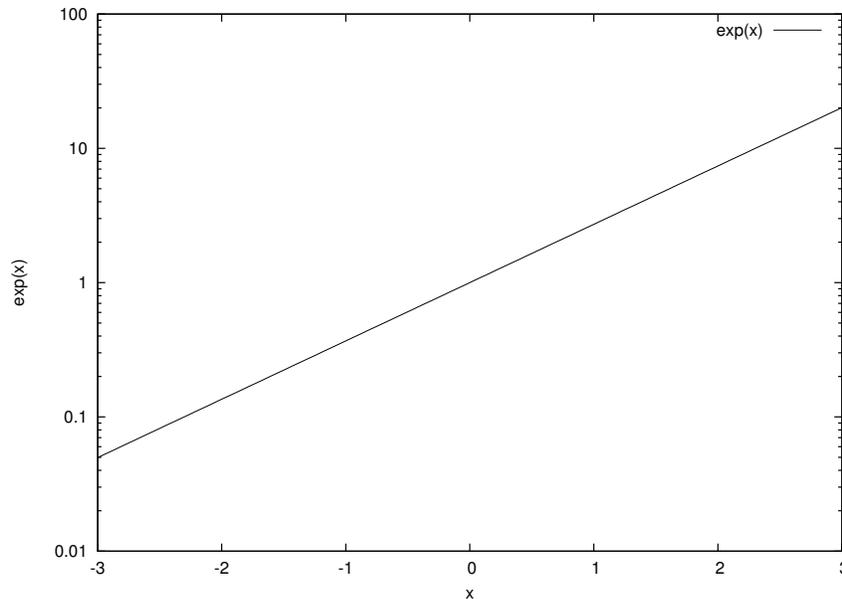

# MODELS FOR CMOS DEVICES

## CMOS (0.25 $\mu\text{m}$ ) – Unified Model.

	$V_{T0}$ (V)	$\gamma$ ( $\text{V}^{0.5}$ )	$V_{DSAT}$ (V)	$k'$ ( $\text{A}/\text{V}^2$ )	$\lambda$ ( $\text{V}^{-1}$ )
NMOS	0.43	0.4	0.63	$115 \times 10^{-6}$	0.06
PMOS	-0.4	-0.4	-1	$-30 \times 10^{-6}$	-0.1

## CMOS (0.25 $\mu\text{m}$ ) – Switch Model ( $R_{eq}$ )

$V_{DD}$ (V)	1	1.5	2	2.5
NMOS ( $\text{k}\Omega$ )	35	19	15	13
PMOS ( $\text{k}\Omega$ )	115	55	38	31

## CMOS (0.25 $\mu\text{m}$ ) – BSIM Model

See Website: <http://bwrc.eecs.berkeley.edu/IcBook>

# VALUES OF MATERIAL AND PHYSICAL CONSTANTS

Name	Symbol	Value	Units
Room temperature	$T$	300 (= 27°C)	K
Boltzman constant	$k$	$1.38 \times 10^{-23}$	J/K
Electron charge	$q$	$1.6 \times 10^{-19}$	C
Thermal voltage	$\phi_T = kT/q$	26	mV (at 300 K)
Intrinsic Carrier Concentration (Silicon)	$n_i$	$1.5 \times 10^{10}$	$\text{cm}^{-3}$ (at 300 K)
Permittivity of Si	$\epsilon_{si}$	$1.05 \times 10^{-12}$	F/cm
Permittivity of $\text{SiO}_2$	$\epsilon_{si}$	$3.5 \times 10^{-13}$	F/cm
Resistivity of Al	$\rho_{Al}$	$2.7 \times 10^{-8}$	$\Omega\text{-m}$
Resistivity of Cu	$\rho_{Cu}$	$1.7 \times 10^{-8}$	$\Omega\text{-m}$
Magnetic permeability of vacuum (similar for $\text{SiO}_2$ )	$\mu_0$	$12.6 \times 10^{-7}$	Wb/Am
Speed of light (in vacuum)	$c_0$	30	cm/nsec
Speed of light (in $\text{SiO}_2$ )	$c_{si}$	15	cm/nsec

# FORMULAS AND EQUATIONS

## Diode

$$I_D = I_S(e^{V_D/\phi_T} - 1) = Q_D/\tau_T$$

$$C_j = \frac{C_{j0}}{(1 - V_D/\phi_0)^m}$$

$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1 - m)} \times [(\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m}]$$

## MOS Transistor

$$V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$$

$$I_D = \frac{k_n W}{2 L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \text{ (sat)}$$

$$I_D = v_{sat} C_{ox} W \left( V_{GS} - V_T - \frac{V_{DSAT}}{2} \right) (1 + \lambda V_{DS}) \text{ (velocity sat)}$$

$$I_D = k_n \frac{W}{L} (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \text{ (triode)}$$

$$I_D = I_S e^{\frac{qV_{GS}}{nkT}} \left( 1 - e^{-\frac{qV_{DS}}{kT}} \right) \text{ (subthreshold)}$$

## Deep Submicron MOS Unified Model

$$I_D = 0 \text{ for } V_{GT} \leq 0$$

$$I_D = k' \frac{W}{L} \left( V_{GT} V_{min} - \frac{V_{min}^2}{2} \right) (1 + \lambda V_{DS}) \text{ for } V_{GT} \geq 0$$

$$\text{with } V_{min} = \min(V_{GT}, V_{DS}, V_{DSAT})$$

$$\text{and } V_{GT} = V_{GS} - V_T$$

## MOS Switch Model

$$R_{eq} = \frac{1}{2} \left( \frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left( 1 - \frac{5}{6} \lambda V_{DD} \right)$$

## Inverter

$$V_{OH} = f(V_{OL})$$

$$V_{OL} = f(V_{OH})$$

$$V_M = f(V_M)$$

$$t_p = 0.69 R_{eq} C_L = \frac{C_L (V_{swing}/2)}{I_{avg}}$$

$$P_{dyn} = C_L V_{DD} V_{swing} f$$

$$P_{stat} = V_{DD} I_{DD}$$

## Static CMOS Inverter

$$V_{OH} = V_{DD}$$

$$V_{OL} = GND$$

$$V_M \approx \frac{r V_{DD}}{1 + r} \text{ with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$\text{with } g \approx \frac{1 + r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 0.69 C_L \left( \frac{R_{eqn} + R_{eqp}}{2} \right)$$

$$P_{av} = C_L V_{DD}^2 f$$

## Interconnect

$$\text{Lumped RC: } t_p = 0.69 RC$$

$$\text{Distributed RC: } t_p = 0.38 RC$$

RC-chain:

$$\tau_N = \sum_{i=1}^N R_i \sum_{j=i}^N C_j = \sum_{i=1}^N C_i \sum_{j=1}^i R_j$$

Transmission line reflection:

$$\rho = \frac{V_{refl}}{V_{inc}} = \frac{I_{refl}}{I_{inc}} = \frac{R - Z_0}{R + Z_0}$$

# CMOS COMBINATIONAL LOGIC

## Transistor Sizing using Logical Effort

$$F = \frac{C_L}{C_{g1}} = \prod_{i=1}^N \frac{f_i}{b_i} \quad G = \prod_{i=1}^N g_i \quad D = t_{p0} \sum_{j=1}^N \left( p_j + \frac{f_j g_j}{\gamma} \right)$$

$$B = \prod_{i=1}^N b_i \quad H = FGB \quad D_{min} = t_{p0} \left( \sum_{j=1}^N p_j + \frac{N(N/H)}{\gamma} \right)$$